


Welcome to
CSE250 Mid Exam (Slot 1)
Date: 20 November, 2021
Duration: 1 Hour + 10 minutes(for PDF)

Rules:

1. Write Your Name and Student ID in the first page of your script.
1. Do not use any any external devices except calculator.
2. **No online resources are allowed**
3. Place your camera in such a way that it shows your face and both hands
4. If you get disconnected from the meet link unintentionally, **you must inform your faculty when you rejoin.**
5. Write your answers and equations **clearly.**
6. After you have finished writing your answers wait for faculty's confirmation before starting to make your pdf.


1. Write down the Nodal equations for Node 1, 2 and 3
2. Find the value of v_o using nodal analysis

Q1

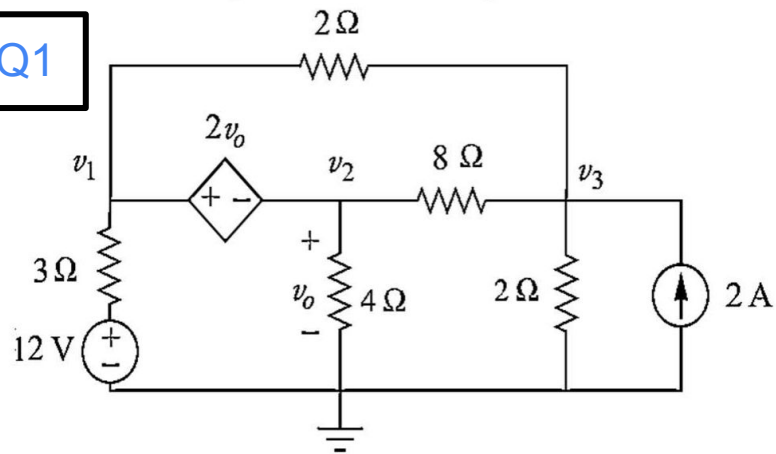


Draw the simplified circuit diagram using Source transformation method, then find the value of v_o

Q2

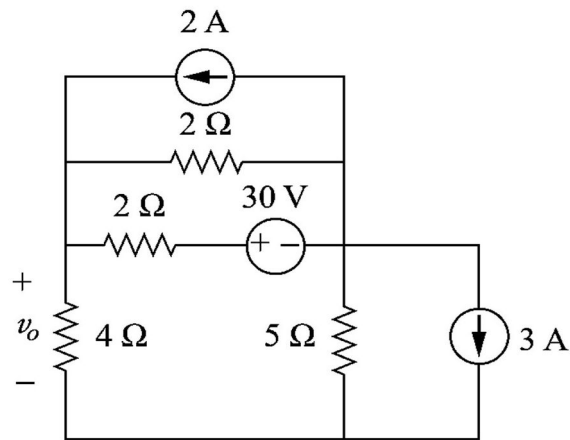

Q3

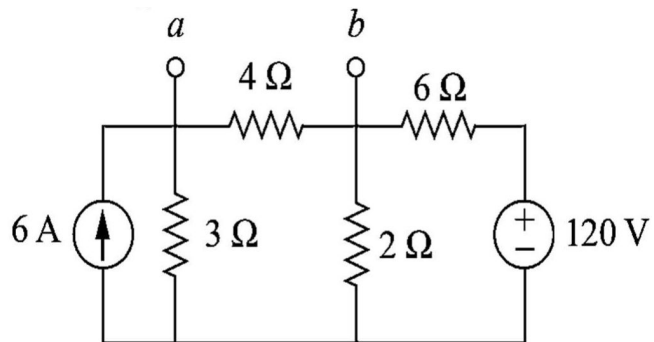

1. What's the value of V_{th} and R_{th} .
2. Draw the thevenin equivalent circuit across the terminal $a-b$.