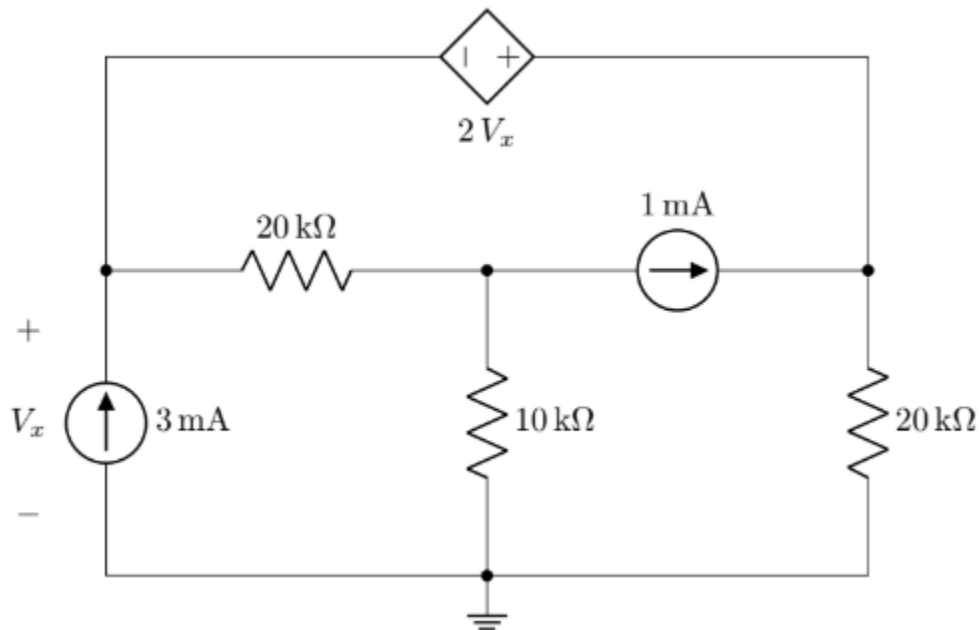


Problems for assignment 2:

- Using mesh analysis to find the power of the dependent voltage source. Do you think nodal analysis would have been easier? If yes, why so? [5 marks]



- Find I_x in the circuit shown above using Nodal analysis. Do you think mesh analysis would have been easier? If yes, why so? [3 marks]
 (b) Which side (top or bottom) of the $2\ \Omega$ resistor on the left has a higher voltage? [1 mark]
 (c) Determine the voltage across the $2 I_x$ dependent current source. [1 mark]

