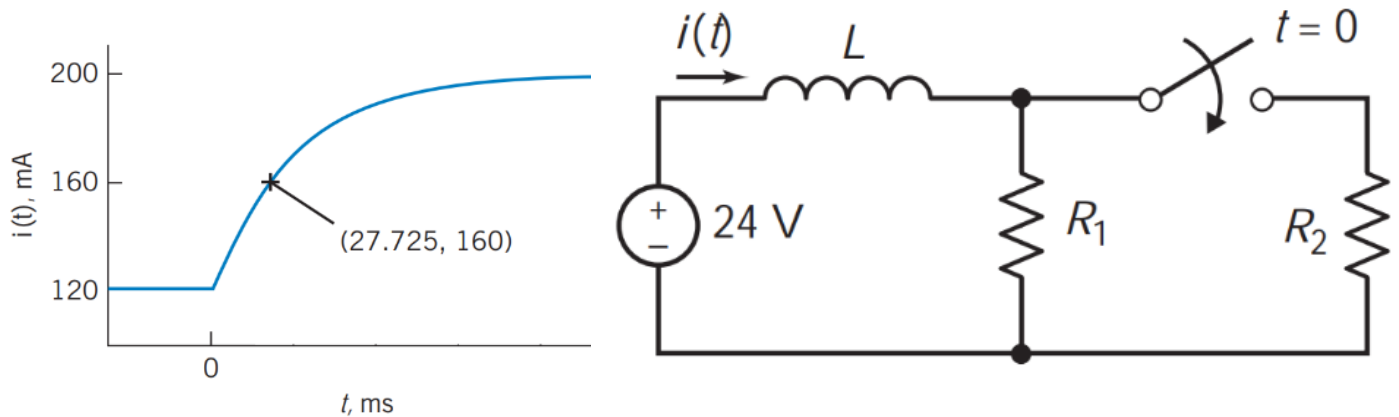


CSE250-10
Summer 26
ASSIGNMENT 4

Deadline: 19 July, 2026
(11:59 pm)

1. The inductor current $i(t)$ has the following plot. Determine the values of L, R_1 and R_2 .



2. Find $v(t)$ for $t > 0$

